

# Lecture 7

Clocking continued

# Quick Review

- Synchronous
- Mesochronous
- Plesiochronous
- Asynchronous

# **GENERAL PURPOSE ASYNCHRONOUS CLOCK CROSSING**

# Observe

- Can build mesochronous and plesiochronous synchronizers with no failure probability

# Asynchronous Clock Crossing

- Most common scenario in ASIC/FPGA design
- Non-zero probability of failure
- Can only reduce probability

# Basics Again



# Crude Exercise






# Crossing 1 Signal

# Solution

# One More Thing


Consider (esp. in FPGAs)

 


C can still see metastability at input  
Why?

# The Fix

# Synchronizer Block

 


# Multiple Control Signals

 


$EN1$  &  $EN2$  Change  
at same time

# Counter

 




# Datapath – Bus

 

Again, multiple  
bits crossing



# FIFO

 

Synch: Write Clock = Read Clock


Rate matching


Asynch: Also for Clock Crossing

Use a dual-ported Asynch  
memory

Asynch memory

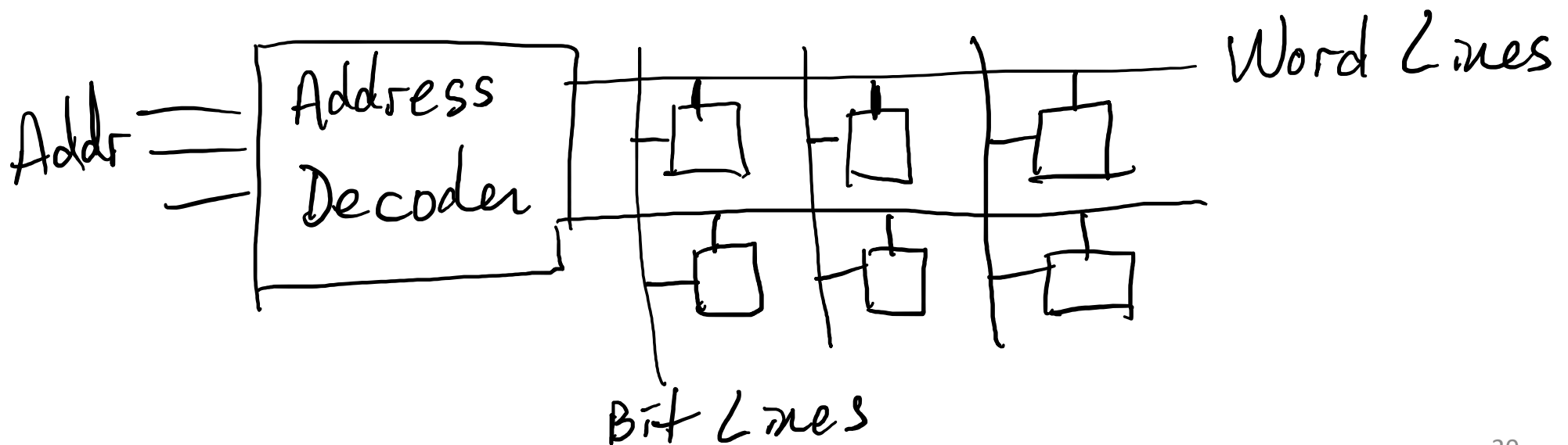- address in  $\rightarrow$  data out
- all combinational



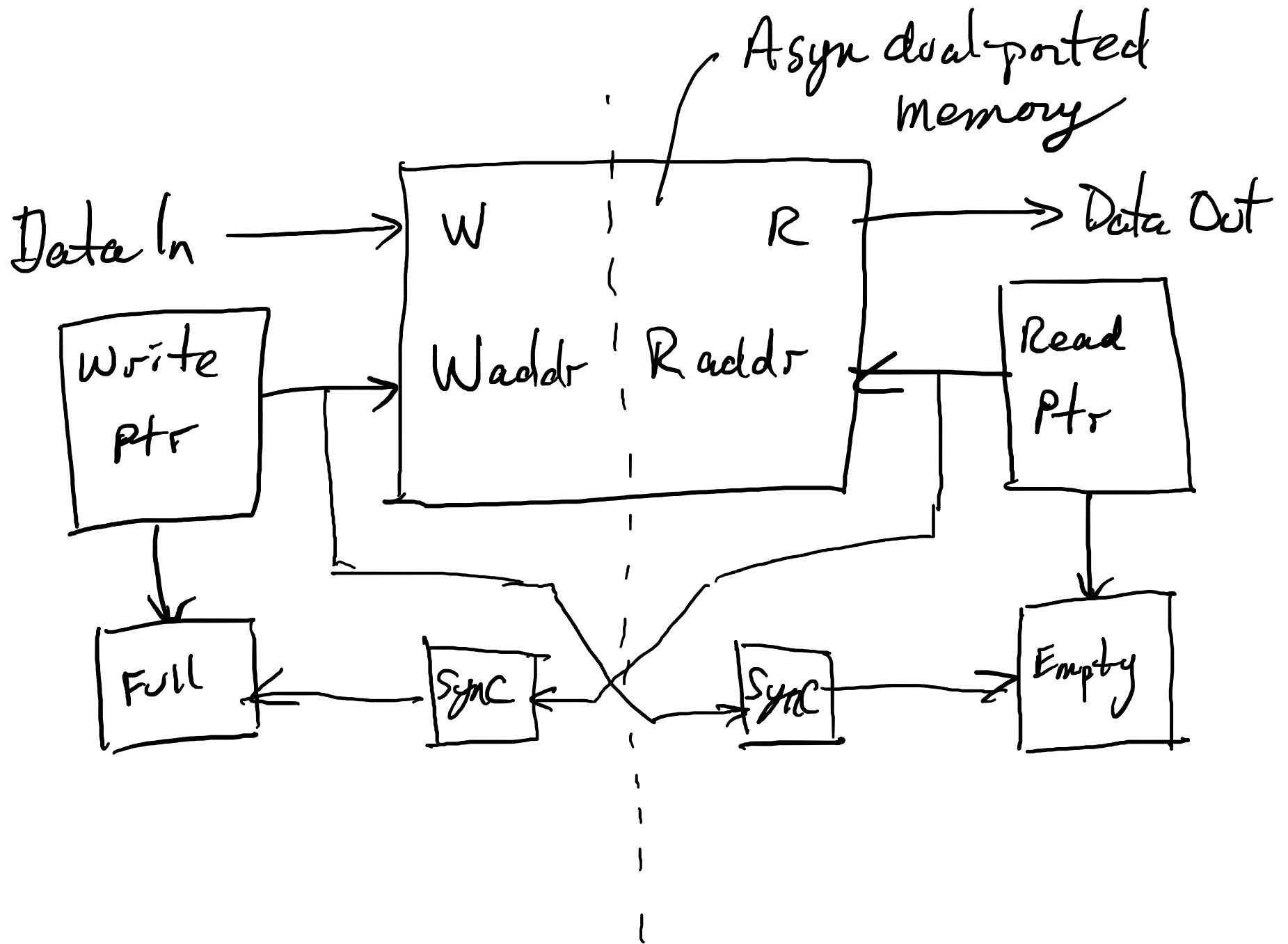


# **STATIC TIMING ANALYSIS (STA)**

# Timing Simulation


# Static Timing Analysis



# False Path

 


# Multi-cycle Path

 

# Constraints and P&R Time

# Timing and Clock Crossing

Synchronizer

 

STA

Simulation

# Style: Partition